

# Verilog Review

Lecture 03

Josh Brake

Harvey Mudd College

# Outline

- Verilog tips
- Design guidelines and basic idioms
- Bad Verilog Examples/Bug finding

# Learning Objectives

By the end of this lecture you should be able to...

- Recall basic Verilog idioms for common digital structures
- Analyze Verilog code to find errors

# Verilog Tips

- Think about \_\_\_\_\_ you want, write code that implies it. Use the \_\_\_\_\_ and never think about this as coding.
- Watch for \_\_\_\_\_ in tool. Take them seriously – often a sign of a big problem.
- \_\_\_\_\_ : draw box with inputs, outputs. Divide into simpler boxes until you can understand it.

# Design Guidelines and Idioms for Common Structures

- Simple combinational logic: use \_\_\_\_\_
- For a mux: \_\_\_\_\_
- Truth tables: always\_comb and \_\_\_\_\_ (default case of x)
- Finite state machines. Three portions: \_\_\_\_\_, \_\_\_\_\_, \_\_\_\_\_.
- Use \_\_\_\_\_, \_\_\_\_\_, not plain always blocks.
- Use \_\_\_\_\_ datatype everywhere except on tristates, and don't use tristates

# System Verilog Operators

Listed in order of descending precedence.

Verilog Operator	Name	Functional Group
[ ]	bit-select or part-select	
( )	parenthesis	
!	logical negation	logical
~	negation	bit-wise
&	reduction AND	reduction
	reduction OR	reduction
~&	reduction NAND	reduction
~	reduction NOR	reduction
^	reduction XOR	reduction
~^ or ^~	reduction XNOR	reduction
+	unary (sign) plus	arithmetic
-	unary (sign) minus	arithmetic
{ }	concatenation	concatenation
{}{}}	replication	replication
*	multiply	arithmetic
/	divide	arithmetic
%	modulus	arithmetic
+	binary plus	arithmetic
-	binary minus	arithmetic

<<	shift left	shift
>>	shift right	shift
>	greater than	relational
>=	greater than or equal to	relational
<	less than	relational
<=	less than or equal to	relational
==	logical equality	equality
!=	logical inequality	equality
==	case equality	equality
!=	case inequality	equality
&	bit-wise AND	bit-wise
^	bit-wise XOR	bit-wise
~^ or ^~	bit-wise XNOR	bit-wise
	bit-wise OR	bit-wise
&&	logical AND	logical
	logical OR	logical
:?	conditional	conditional

# Bad Verilog: Learning by Counter Example

# Bad Verilog Example #1

```
1 module mux(input logic [3:0] d0, d1,
2             input logic      s,
3             output logic [3:0] y);
4     always_comb @ (posedge s)
5         if (s) y <= d1;
6         else   y <= d0;
7 endmodule
```

# Bad Verilog Example #2

```
1 module mux2(input logic [3:0] d0, d1,
2               input logic      s,
3               output      [3:0] y);
4
5   tristate t0(d0, s, y);
6   tristate t1(d1, s, y);
7 endmodule
```

# Bad Verilog Example #3

```
1 module mux3(input logic [3:0] d0, d1, d2,
2             input logic [1:0] s,
3             output logic [3:0] y);
4
5   always_comb
6     if (s == 2'b00) y <= d0;
7     else if (s == 2'b01) y <= d1;
8     else if (s == 2'b10) y <= d2;
9   endmodule
```

# Bad Verilog Example #4

```
1 module mux8(input logic [3:0] d0, d1, d2, d3, d4, d5, d6, d7,
2               input logic [2:0] s,
3               output logic [3:0] y);
4
5   always_comb
6     case (s)
7       1'd0: y <= d0;
8       1'd1: y <= d1;
9       1'd2: y <= d2;
10      1'd3: y <= d3;
11      1'd4: y <= d4;
12      1'd5: y <= d5;
13      1'd6: y <= d6;
14      1'd7: y <= d7;
15      default: y <= 4'bxxxx;
16   endcase
17 endmodule
```

# Bad Verilog Example #5

```
1 module and3(input logic a, b, c,
2             output logic y);
3
4     logic tmp;
5
6     always @(a, b, c)
7     begin
8         tmp <= a & b;
9         y <= tmp & c;
10    end
11 endmodule
```

# Bad Verilog Example #6

```
1 module counter(input logic      clk,
2                  output logic [31:0] q);
3
4   always_ff @(posedge clk)
5     q <= q+1;
6 endmodule
```

# Bad Verilog Example #7

```
1 module counter2(input logic clk,
2                  output logic [31:0] q);
3   initial q <= 32'b0;
4
5   always_ff @(posedge clk) q <= q+1;
6 endmodule
```

# Bad Verilog Example #8

```
1 module gates(input logic [3:0] a, b,
2               output logic [3:0] y1, y2, y3, y4, y5);
3
4   always @(a)
5     begin
6       y1 <= a & b; // AND
7       y2 <= a | b; // OR
8       y3 <= a ^ b; // XOR
9       y4 <= ~(a & b); // NAND
10      y5 <= ~(a | b); // NOR
11    end
12 endmodule
```

# Bad Verilog Example #9

```
1 module priority_always(input logic [3:0] a,
2                         output logic [3:0] y);
3
4     // a 4-input priority encoder
5     always_comb
6         if      (a[3]) y <= 4'b1000;
7         else if (a[2]) y <= 4'b0100;
8         else if (a[1]) y <= 4'b0010;
9         else if (a[0]) y <= 4'b0001;
10    endmodule
```

# Bad Verilog Example #10

```
1 module seven_seg_display_decoder(input logic [3:0] data,
2                                     output logic [6:0] segments);
3     always_comb
4         case (data)
5             0: segments <= 7'b000_0000; // ZERO
6             1: segments <= 7'b111_1110; // ONE
7             2: segments <= 7'b011_0000; // TWO
8             3: segments <= 7'b110_1101; // THREE
9             4: segments <= 7'b011_0011; // FOUR
10            5: segments <= 7'b101_1011; // FIVE
11            6: segments <= 7'b101_1111; // SIX
12            7: segments <= 7'b111_0000; // SEVEN
13            8: segments <= 7'b111_1111; // EIGHT
14            9: segments <= 7'b111_1011; // NINE
15        endcase
16    endmodule
```

# Bad Verilog Example #11

```
1 module latch(input logic      clk,
2               input logic [3:0] d,
3               output logic [3:0] q);
4
5   always_latch @(clk)
6     if (clk) q <= d;
7 endmodule
```

# Bad Verilog Example #12

```
1 module flopren(input logic      clk,
2                  input logic      reset,
3                  input logic      set,
4                  input logic [3:0] d,
5                  output logic [3:0] q);
6
7   always_ff @(posedge clk, posedge reset)
8     if (reset) q <= 0;
9     else       q <= d;
10
11  always @ (set)
12    if (set) q <= 1;
13 endmodule
```

# Bad Verilog Example #13

```
1 module twobitflop(input logic      clk,
2                     input logic [1:0] d,
3                     output logic [1:0] q);
4
5   always_ff @(posedge clk)
6     q[1] = d[1];
7     q[0] = d[0];
8 endmodule
```

# Bad Verilog Example #14

```
1 module FSMbad(input logic clk,
2                 input logic a,
3                 output logic out1, out2);
4
5     logic state;
6
7     always_ff @(posedge clk)
8         if (state == 0) begin
9             if (a) state <= 1;
10            end else begin
11                if (~a) state <= 0;
12            end
13
14        always_comb
15            if (state == 0) out1 <= 1;
16            else           out2 <= 1;
17    endmodule
```

# Bad Verilog Example #15

```
1 module divideby3counter(input logic      clk, reset,
2                           output logic [1:0] q);
3
4   always_ff @(posedge clk or posedge reset)
5     if (reset) q = 0;
6     else begin
7       q = q+1;
8       if (q == 2) q = 0;
9     end
10  endmodule
```

# Bad Verilog Example #16

```
1 module divideby3FSM(input logic clk,
2                      input logic reset,
3                      output logic out);
4
5   logic [1:0] state, nextstate;
6
7   parameter S0 = 2'b00;
8   parameter S1 = 2'b01;
9   parameter S2 = 2'b10;
10
11  // State Register
12  always_ff @(posedge clk, posedge reset)
13    if (reset) state <= S0;
14    else      state <= nextstate;
15 // Next State Logic
16  always_comb
17    case (state)
18      S0: nextstate <= S1;
19      S1: nextstate <= S2;
20      S2: nextstate <= S0;
21    endcase
22
23  // Output Logic
24  assign out = (state == S2);
25 endmodule
```

# Bad Verilog Example #17

```
1 module divideby3FSM2(input logic clk,
2                      output logic out);
3
4   logic [1:0] state, nextstate;
5
6   parameter S0 = 2'b00;
7   parameter S1 = 2'b01;
8   parameter S2 = 2'b10;
9
10  initial state = 2'b00;
11
12  // State Register
13  always_ff @(posedge clk)
14    if (state == 2'b00) state <= 2'b01;
15    else if (state == 2'b01) state <= 2'b10;
16    else if (state == 2'b10) state <= 2'b00;
17
18  // Output Logic
19  assign out = (state == S2);
20 endmodule
```

# Bad Verilog Example #18

```
1 module adventuregameFSM(input          clk, reset, N, S, E, W,
2                           output logic [3:0] room,
3                           output logic      win, die);
4
5   always_ff @(posedge clk or posedge reset)
6     if (reset) begin
7       room <= 4'b0001;
8       die  <= 0;
9       win   <= 0;
10    end
11
12   else case (room)
13     4'b0001: if (E) room <= 4'b0010;
14       else die  <= 1;
15     4'b0010: if (S) room <= 4'b0100;
16       if (W) room <= 4'b0001;
17       else die  <= 1;
18     4'b0100: if (E) room <= 4'b1000;
19       if (N) room <= 4'b0010;
20       else die  <= 1;
21   endcase
22   always_comb
23     if (room == 4'b1000) win <= 1;
24 endmodule
```

# Wrap Up

- Think about hardware you want. Then write the HDL to imply the proper logic.
- Check the Netlist Analyzer to ensure that the tool is inferring the logic you are intending.
- Make sure to not infer latches.

# Announcements and Reminders